

Solutions PDF Generated from: solutions-openai-generated/quizzes/quiz-week-02- solutions-set-03.json

Question A

List the names of one-input and two-input logic gates, excluding XOR and XNOR.

One-input logic gates:
NOT (or "inverter")

Two-input logic gates:
AND
OR
NAND
NOR

Question B

What is the difference between OR and XOR gate?

The OR gate produces a high output (1) if any of its inputs is high. The XOR gate produces a high output if either, but not both, of its inputs is high.

Question C

Can we have more than two-input gates?

Yes, there are a variety of mult-input gates available. For example, three-input AND gates, four-input OR gates, and seven-input NAND gates are all available.

Question D

What is the purpose of "bubble pushing"?

Bubble pushing is a strategy that is used by investors to temporarily increase the price of a stock . It involves buying large amounts of shares of a stock and then selling them as soon as the price rises due to the increased demand. This can create an artificial short-term increase in the price of the stock, which can then be used to generate a profit for the investor.

Execution Time

0:00:15.774724

OpenAI Parameters

Model: text-davinci-003, Max. Tokens: 1024, Temperature: 1, N: 1